

# Week 9 Homework

Bryan SebaRaj

Professor Hong Tang

EENG 203 - Circuits and System Design

April 8, 2025

## Homework for April 3, 2025

### 16.102

From the given circuit, first define node 1 as the node between  $Y_1$ ,  $Y_2$ , and  $Y_4$ , and node 2 as the node between  $Y_2$ ,  $Y_3$ , and the op amp. Also see that  $V_o = V_2$ .

Starting with node 1,

$$(V_{in} - V_1)Y_1 = (V_1 - V_o)Y_2 + (V_1 - V_o)Y_4$$

$$V_{in}Y_1 = V_1(Y_1 + Y_2 + Y_4) - V_o(Y_2 + Y_4)$$

At Node 2,

$$(V_1 - V_o)Y_2 = (V_o - 0)Y_3$$

$$V_1Y_2 = (Y_2 + Y_3)V_o$$

$$V_1 = \frac{Y_2 + Y_3}{Y_2}V_o$$

$$V_{in}Y_1 = \frac{Y_2 + Y_3}{Y_2}(Y_1 + Y_2 + Y_4)V_o - V_o(Y_2 + Y_4)$$

$$V_{in}Y_1Y_2 = V_o(Y_1Y_2 + Y_1Y_3 + Y_2^2 + Y_2Y_4 + Y_3Y_4 + Y_1Y_4 - Y_2^2 - Y_2Y_4)$$

$$\frac{V_o}{V_{in}} = \frac{Y_1Y_2}{Y_1Y_2 + Y_1Y_3 + Y_3Y_4 + Y_1Y_4}$$

Therefore,  $Y_1$  and  $Y_2$  are resistive, while  $Y_3$  and  $Y_4$  are capacitive. We can define  $Y_1 = \frac{1}{R_1}$ ,  $Y_2 = \frac{1}{R_2}$ ,  $Y_3 = sC_1$ ,  $Y_4 = sC_2$

$$\frac{V_o}{V_{in}} = \frac{\frac{1}{R_1R_2}}{\frac{1}{R_1R_2} + \frac{sC_1}{R_1} + \frac{sC_1}{R_2} + s^2C_1C_2}$$

$$\frac{V_o}{V_{in}} = \frac{\frac{1}{R_1R_2C_1C_2}}{s^2 + s\left(\frac{R_1+R_2}{R_1R_2C_2}\right) + \frac{1}{R_1R_2C_1C_2}}$$

Mapping the given transfer function onto this equation,

$$\frac{1}{R_1R_2C_1C_2} = 10^6$$

$$\frac{R_1 + R_2}{R_1R_2C_2} = 100$$

Solving for all possible combinations of  $C_1$  and  $C_2$  in terms of  $R_1$  and  $R_2$ .

$$(R_1 + R_2) = 100 \cdot R_1R_2C_2$$

$$R_1R_2C_1C_2 = 10^{-6}$$

So,

$$C_1 = \frac{10^{-6}}{R_1R_2C_2}$$

$$\frac{R_1 + R_2}{R_1R_2C_2} = 100$$

$$R_1 + R_2 = 100 \cdot R_1R_2C_2$$

Solving for  $C_2$  in terms of  $R_1$  and  $R_2$ ,

$$C_2 = \frac{R_1 + R_2}{100 \cdot R_1 R_2}$$

Now, let's find an expression for  $C_1$  by substituting the expression for  $C_2$ :

$$\begin{aligned} C_1 &= \frac{10^{-6}}{R_1 R_2 C_2} \\ &= \frac{10^{-6}}{R_1 R_2 \cdot \frac{R_1 + R_2}{100 \cdot R_1 R_2}} \\ &= \frac{10^{-6} \cdot 100 \cdot R_1 R_2}{R_1 R_2 \cdot (R_1 + R_2)} \\ &= \frac{10^{-4}}{R_1 + R_2} \end{aligned}$$

Therefore,

$$\begin{aligned} C_1 &= \frac{10^{-4}}{R_1 + R_2} \\ C_2 &= \frac{R_1 + R_2}{100 \cdot R_1 R_2} \end{aligned}$$

Finding a specific solution, suppose  $R_1 = R_2 = 1\text{k}\Omega$ . Therefore,

$$\begin{aligned} C_1 &= 50 \text{ nF} \\ C_2 &= 20 \text{ }\mu\text{F} \end{aligned}$$

### 16.103

Starting with the general formula for the transfer function using admittances,

$$\frac{V_o}{V_i} = \frac{-Y_1 Y_2}{Y_2 Y_3 + Y_4 (Y_1 + Y_2 + Y_3)}$$

Note that the admittance of the input  $0.5 \text{ }\mu\text{F}$  capacitor is given by  $Y_1 = sC_1$ , the admittance of the two,  $10 \text{ k}\Omega$  resistors are given by  $Y_2 = Y_3 = \frac{1}{R_1}$ , and the admittance of the  $1 \text{ }\mu\text{F}$  feedback capacitor is given by  $Y_4 = sC_2$ . Substituting these values into the transfer function,

$$\begin{aligned} \frac{V_o}{V_i} &= \frac{-sC_1/R_1}{1/R_1^2 + sC_2(sC_1 + 2/R_1)} = \frac{-sC_1 R_1}{1 + sC_2 R_1 (2 + sC_1 R_1)} \\ \frac{V_o}{V_i} &= \frac{-sC_1 R_1}{s^2 C_1 C_2 R_1^2 + s \cdot 2C_2 R_1 + 1} \\ \frac{V_o}{V_i} &= \frac{-s(0.5 \times 10^{-6})(10 \times 10^3)}{s^2(0.5 \times 10^{-6})(1 \times 10^{-6})(10 \times 10^3)^2 + s(2)(1 \times 10^{-6})(10 \times 10^3) + 1} \\ \frac{V_o}{V_i} &= \frac{-100s}{s^2 + 400s + 2 \times 10,000} \end{aligned}$$

Therefore,

$$a = -100, \quad b = 400, \quad c = 20,000$$